

● Task2:

Using LIPO battery is useful that it offers high capacity and hence can be used to hold more power.

To calculate the current through the LED Using ohm law ($v=iR$)

$$I = V/R = 12V/3.3\Omega = 3.64A$$

to estimate the battery life, we divide the total battery capacity(5200mAh) by the current consumption (3.64A) to get the approximate runtime in hours

$$\text{Battery life} = \text{Battery capacity} / \text{current consumption} = 5200\text{mAh} / 3.64A = 1.428h$$

(SO SINGLE LIPO BATTERY IS NOT SUFFICIENT)

$$\text{Number of batteries} = \text{desired time} / \text{Battery life} = 5 / 1.43 = 3.5 \text{ batteries}$$

since we can not use a fraction number of a battery, we round it to the nearest number.it means that we need **at least 4 batteries** connected in parallel for more than 5 hours.